



भारतीय प्रौद्योगिकी संस्थान गांधीनगर
पालज, गांधीनगर, गुजरात 382 055

INDIAN INSTITUTE OF TECHNOLOGY GANDHINAGAR
PALAJ, GANDHINAGAR, GUJARAT 382 055

Name : Bhavik Patel
Roll no. : 22110047

IITGN

Digital Systems LAB -8

Question:

You have designed a parallel register where all the bits are simultaneously loaded into the register. In this lab, we will make a register file (where there are several registers).

Design 32-bit register file with 8 registers. Name these registers as R0, R1, ..R7. The register file allows moving contents of one register to another. The source and destination registers are given in the testbench.

For example, MOV R0, R1 is like saying move the contents of Register-1 to Register-0.

Verilog Code for 8 32-bit registers

```
`timescale 1ns / 1ps
module bit32Register(rst,D,clk,src,dest);
input rst,clk;
input [255:0]D;
input [2:0]src,dest;
reg [31:0]out[7:0];
integer i;
always @(*)
begin
    if(rst) begin
        out[0]<=D[31:0];
        out[1]<=D[63:32];
        out[2]<=D[95:64];
        out[3]<=D[127:96];
        out[4]<=D[159:128];
        out[5]<=D[191:160];
        out[6]<=D[223:192];
        out[7]<=D[255:224];
    end
end

always @(posedge clk) begin
    if(~rst) begin
        out[dest]<=out[src];
    end
end
endmodule
```

We have an rst (reset) input; if it is high, we initialize all 8 registers with some input given in the test bench.

We will store the registers as a 2-D array.

At the posedge of clk we will parallelly load the value in src(source) register to dest(destination) register.

Registers are encoded as

R0=3'b000

R1=3'b001

R2=3'b010

R3=3'b011

R4=3'b100

R5=3'b101

R6=3'b110

R7=3'b111

Test bench

```
`timescale 1ns / 1ps

module test_bench();
  reg rst,clk;
  reg [2:0]src,dest;
  reg [255:0]D;
  integer i;
  bit32Register uut(rst,D,clk,src,dest);

  initial begin
    ○   clk=0;
    ○   forever #5 clk=~clk;
  end

  initial
  begin
    ○   rst=1;
        //Initialise the registers
    ○   D=0;
    ○   for(i=0; i<256;i=i+33) begin
    ○     D[i]=1;
        end
    ○   src=3'b000;
    ○   dest=3'b000;
    ○   D<=D;
    ○   #10;
    ○   rst=0;


    ○   src=3'b000;
    ○   dest=3'b111;
    ○   #10;

    ○   src=3'b010;
    ○   dest=3'b011;
    ○   #10;

    ○   src=3'b110;
    ○   dest=3'b001;
    ○   #10;
  end
endmodule
```

NOTE: Parallel loading of one register to another register will happen at the posedge of the clock signal.

Simulation

 

1. First we have reset high so that we can initialize the registers.
2. Then we make rst=0 and at the first posedge of the clk we have src=0 and dest=7 which means we need to load or copy the content of register 0 to register 7
3. We could see that the value stored in register 0 which is 1 is copied to register 7 at the posedge of the clock.
4. Similar operations are carried out in the next inputs of the test bench also which can be verified from the simulation results.