



भारतीय प्रौद्योगिकी संस्थान गांधीनगर
पालज, गांधीनगर, गुजरात 382 055

INDIAN INSTITUTE OF TECHNOLOGY GANDHINAGAR
PALAJ, GANDHINAGAR, GUJARAT 382 055

Name : Bhavik Patel
Roll no. : 22110047

IITGN

Digital Systems LAB -10

Question:

Implement a Moore and Mealy machine that can detect 10010. The FSM has one input and one output. Show the implemented designs on FPGA. The pattern should be given through a switch and the output should be shown on the LED (which can turn on when the pattern is detected).

Moore Machine Verilog Code

```
`timescale 1ns / 1ps
module Moore_10010(clk,rest,w,z);
input clk,rest,w;
output z;
reg [2:0]y,Y;

parameter [2:0]A=3'b000,B=3'b001,C=3'b010,D=3'b011,E=3'b100,F=3'b101;


//Define the next state combinational logic
always @(w or y)
    case(y)
        A: if(w) Y=B;
            else Y=A;
        B: if(w) Y=B;
            else Y=C;
        C: if(w) Y=B;
            else Y=D;
        D: if(w) Y=E;
            else Y=A;
        E: if(w) Y=B;
            else Y=F;
        F: if(w) Y=B;
            else Y=D;
        default: Y=2'bxx;
    endcase

//Define sequential block
always @(negedge rest or posedge clk)
    if(rest==0)
        y<=A;
    else
        y<=Y;

//Define output
assign z=(y[0] && (~y[1]) && y[2]);

endmodule
```

Simulation of Moore Machine

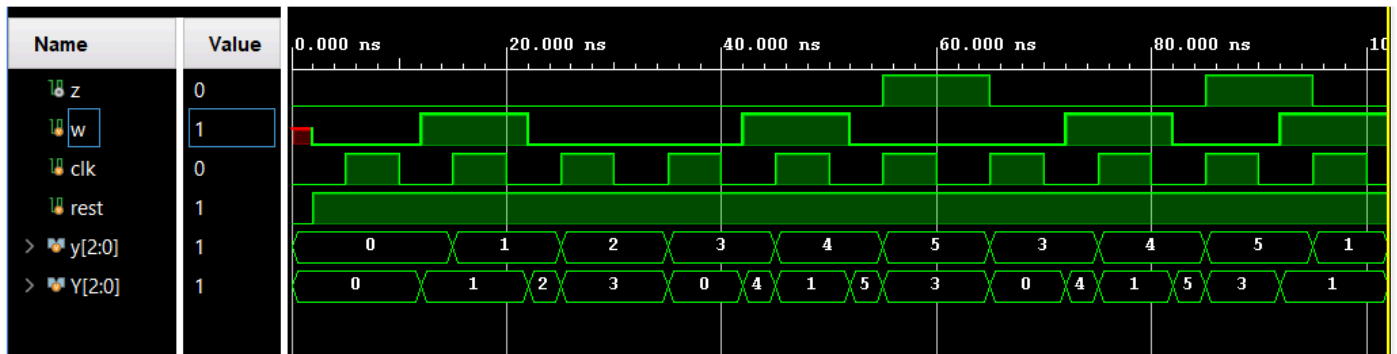

FPGA Implementation:

Link to→[Video](#)

Reports:

Timing Report	
Slack:	inf
Source:	y_reg[0]/C (rising edge-triggered cell FDCE)
Destination:	z (output port)
Path Group:	(none)
Path Type:	Max at Slow Process Corner
Data Path Delay:	7.945ns (Logic 4.085ns (51.413%) route 3.860ns (48.587%))
Logic Levels:	3 (FDCE=1 LUT3=1 OBUF=1)

On-Chip	Power (W)	Used	Available	Utilization (%)
Slice Logic	0.053	48	---	---
LUT as Logic	0.019	4	20800	0.02
CARRY4	0.016	7	8150	0.09
Register	0.013	31	41600	0.07
BUFG	0.006	1	32	3.13
Others	0.000	3	---	---
Signals	0.095	43	---	---
I/O	0.905	5	106	4.72
Static Power	0.074			
Total	1.127			

1. Slice Logic					
Site Type	Used	Fixed	Available	Util%	
Slice LUTs	4	0	20800	0.02	
LUT as Logic	4	0	20800	0.02	
LUT as Memory	0	0	9600	0.00	
Slice Registers	31	0	41600	0.07	
Register as Flip Flop	31	0	41600	0.07	
Register as Latch	0	0	41600	0.00	
F7 Muxes	0	0	16300	0.00	
F8 Muxes	0	0	8150	0.00	

Mealy Machine Verilog Code

```
`timescale 1ns / 1ps
module Mealy_10010(clk,rest,w,z);
input clk,rest,w;
output reg z;
reg [2:0]y,Y;


parameter [2:0]A=3'b000,B=3'b001,C=3'b010,D=3'b011,E=3'b100;

//Define the next state combinational logic
always @(w or y) begin
    case(y)
        A: if(w) begin
            Y=B;z=0;
        end
        else begin
            Y=A;z=0;
        end
        B: if(w) begin
            Y=B;z=0;
        end
        else begin
            Y=C;z=0;
        end
        C: if(w) begin
            Y=B;z=0;
        end
        else begin
            Y=D;z=0;
        end
        D: if(w) begin
            Y=E;z=0;
        end
        else begin
            Y=A;z=0;
        end
    end
end
```

```
E: if(w) begin
    Y=B;z=0;
end
else begin
    Y=C;z=1;
end
default:begin Y=2'bxx; z=0; end
endcase
end

//Define sequential block
always @(negedge rest or posedge clk)
    if(rest==0) begin
        y<=A;z=0; end
    else
        y<=Y;
endmodule
```

Simulation for Mealy Machine

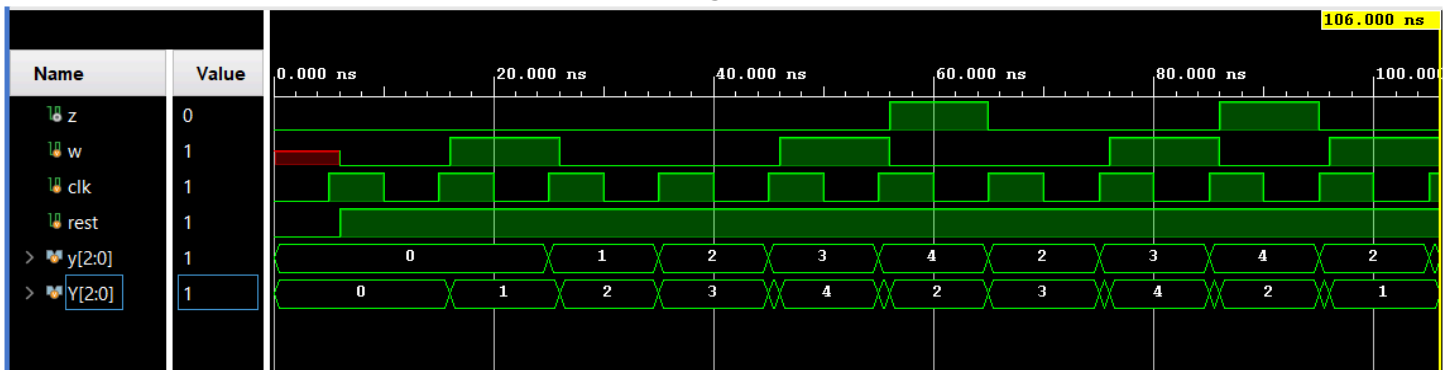

FPGA Implementation:

Link to → [Video](#)

Reports

On-Chip	Power (W)	Used	Available	Utilization (%)
Slice Logic	0.064	48	---	---
LUT as Logic	0.029	4	20800	0.02
CARRY4	0.016	7	8150	0.09
Register	0.013	31	41600	0.07
BUFG	0.006	1	32	3.13
Others	0.000	3	---	---
Signals	0.095	43	---	---
I/O	0.850	5	106	4.72
Static Power	0.074			
Total	1.083			

Timing Report	
Slack:	inf
Source:	inst2/counter_reg[27]/C (rising edge-triggered cell FDRE)
Destination:	slow_clk (output port)
Path Group:	(none)
Path Type:	Max at Slow Process Corner
Data Path Delay:	8.790ns (logic 4.039ns (45.955%) route 4.751ns (54.045%))
Logic Levels:	2 (FDRE=1 OBUF=1)

1. Slice Logic					

Site Type	Used	Fixed	Available	Util%	
Slice LUTs	4	0	20800	0.02	
LUT as Logic	4	0	20800	0.02	
LUT as Memory	0	0	9600	0.00	
Slice Registers	31	0	41600	0.07	
Register as Flip Flop	31	0	41600	0.07	
Register as Latch	0	0	41600	0.00	
F7 Muxes	0	0	16300	0.00	
F8 Muxes	0	0	8150	0.00	

Test bench

For Moore Machine

```
`timescale 1ns / 1ps
module test_tb();
  wire z;
  reg w,clk,rest;

  Moore_10010 uut(clk,rest,w,z);
  initial
  begin
    clk=0;
    forever #5 clk=~clk;
  end

  initial
  begin
    rest=0;
    #2 rest=1;
    w=0;#10
    w=1;#10
    w=0;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=1;#10
    →$finish();
  end
endmodule
```

For Mealy Machine

```
`timescale 1ns / 1ps
module test_tb();
  wire z;
  reg w,clk,rest;

  Mealy_10010 uut(clk,rest,w,z);
  initial
  begin
    clk=0;
    forever #5 clk=~clk;
  end

  initial
  begin
    rest=0;
    #6 rest=1;
    w=0;#10
    w=1;#10
    w=0;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=1;#10
    w=0;#10
    w=1;#10
    →$finish();
  end
endmodule
```